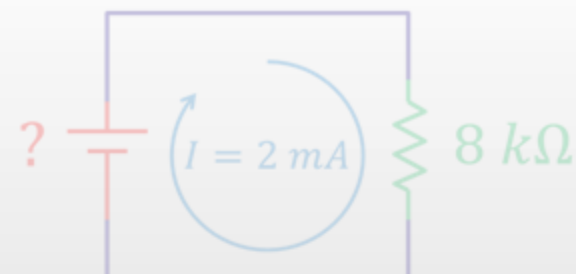




$$I = \frac{V}{R} = \frac{10\text{ V}}{10\ \Omega} = 1\text{ A}$$




$$R = \frac{V}{I} = \frac{10\text{ V}}{2\text{ mA}} = 5\text{ k}\Omega$$




$$V = IR = 2\text{ mA} \cdot 8\text{ k}\Omega = 16\text{ V}$$

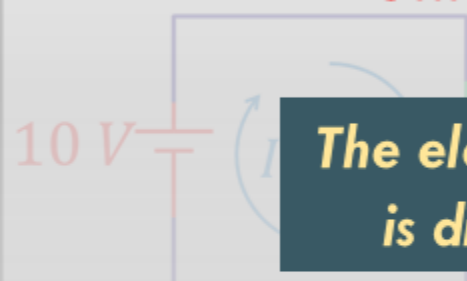
## Ohm's Law Electrical Engineering XYZ Slides


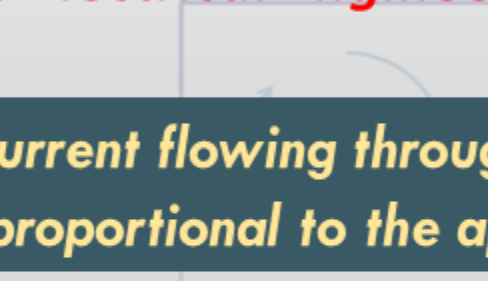
$$I = \frac{V}{R} = \frac{10\text{ V}}{20\ \Omega} = 0.5\text{ A}$$



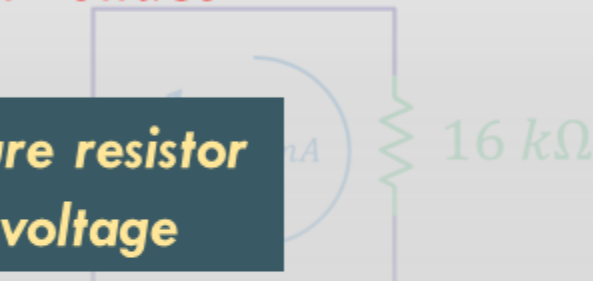
$$R = \frac{V}{I} = \frac{10\text{ V}}{10\text{ mA}} = 1\text{ k}\Omega$$



$$V = IR = 1\text{ mA} \cdot 16\text{ k}\Omega = 16\text{ V}$$

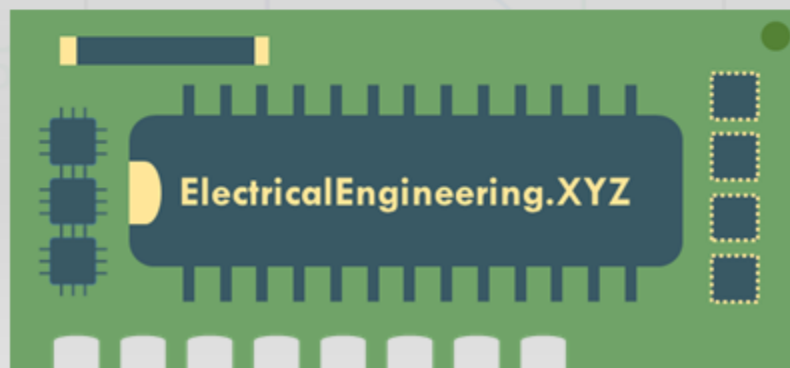The electric current flowing through a pure resistor is directly proportional to the applied voltage








# Ohm's Law



# Ohm's Law

ElectricalEngineering.XYZ

*In this ElectricalEngineering.XYZ Lecture  
You'll learn*

-  **History of Ohm's Law**
-  **Statement of Ohm's Law**
-  **Circuit diagram of Ohm's Law**
-  **Formula of Ohm's Law**
-  **Ohm's law in series circuits**
-  **Ohm's law in parallel circuits**
-  **Ohm's law graphical representation**

[www.electricalengineering.xyz](http://www.electricalengineering.xyz)


# History of Ohm's Law


Georg Simon Ohm was a German who began his research as a school teacher

Using his own created equipment, he founded the direct proportionality relationship between the potential difference (voltage) applied across a conductor and the resultant electric current. This relationship is known as Ohm's law



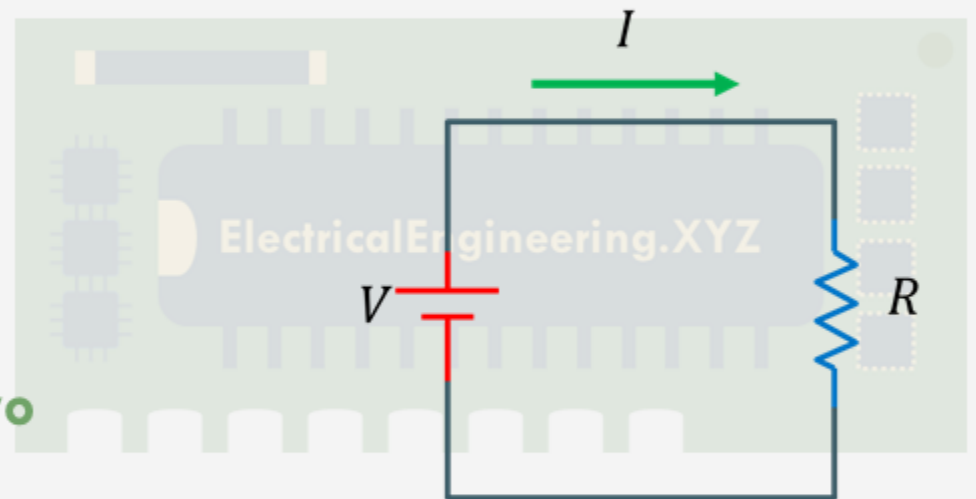
# Statement

 Ohm's law states that the electric current passing through a conductor is directly proportional to the potential difference (voltage) across the two points





$$V = IR$$

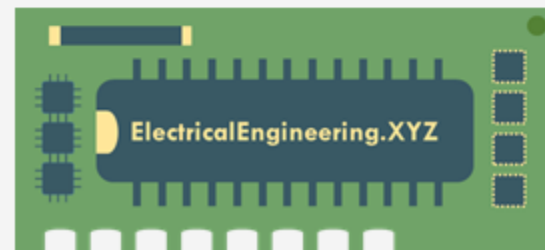

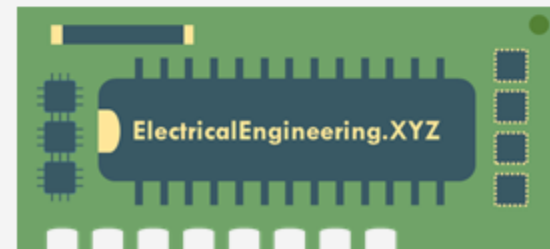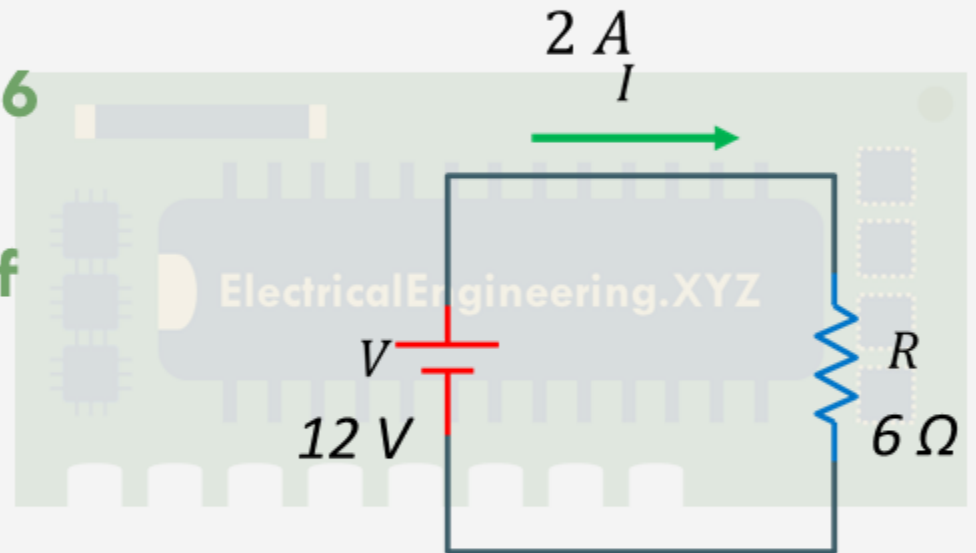
# An Example


The 12 V source connected across a 6 ohms resistor will produce a current of 2 A in the circuit

$$V = IR$$
$$12 \text{ V} = 2 \text{ A} * 6 \Omega$$
$$12 \text{ V} = 12 \text{ V}$$



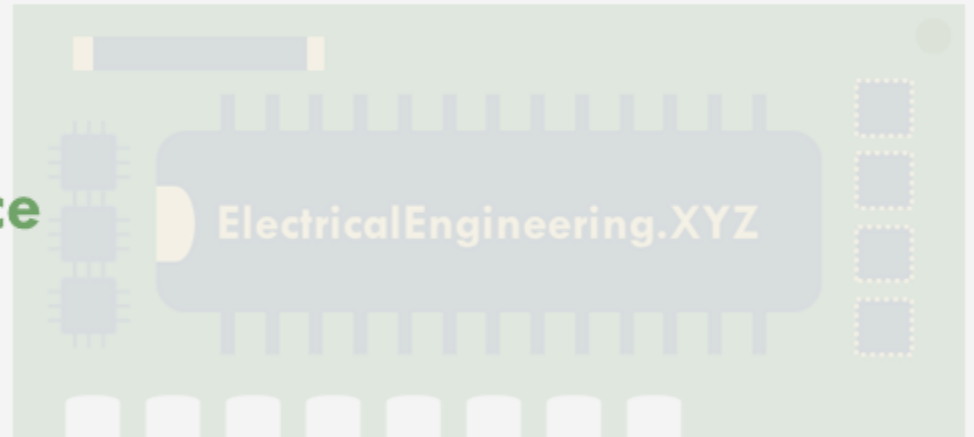
# Ohm's Law and Circuit Analysis

 Ohm's law can be used to determine either current, voltage or resistance provided that other two quantities are known



## Circuit Analysis


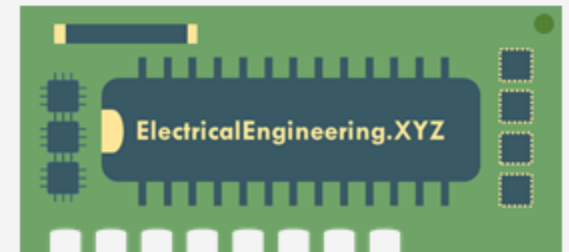


# Ohm's Law and Circuit Analysis

Let's reconsider the circuit provided earlier

Here we have a 6 ohms resistor at our disposal, If we want to calculate the current flow due to 12 V source. We can use Ohm's Law for that

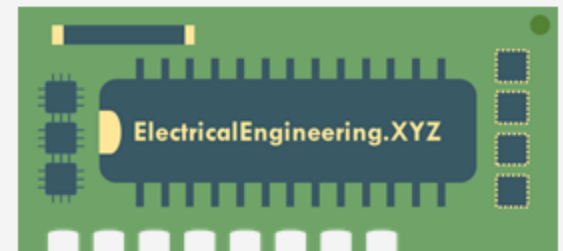
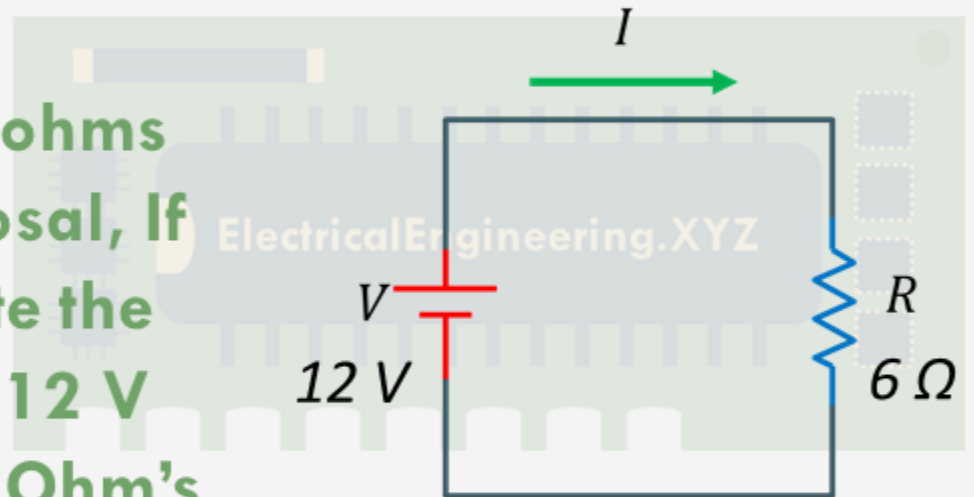
$$I = \frac{V}{R} = \frac{12 V}{6 \Omega} = 2A$$


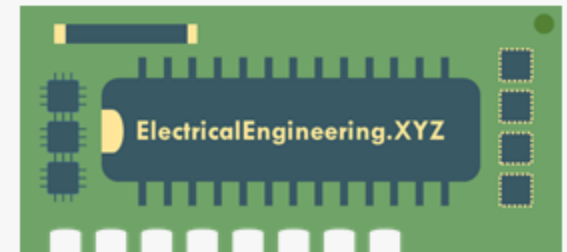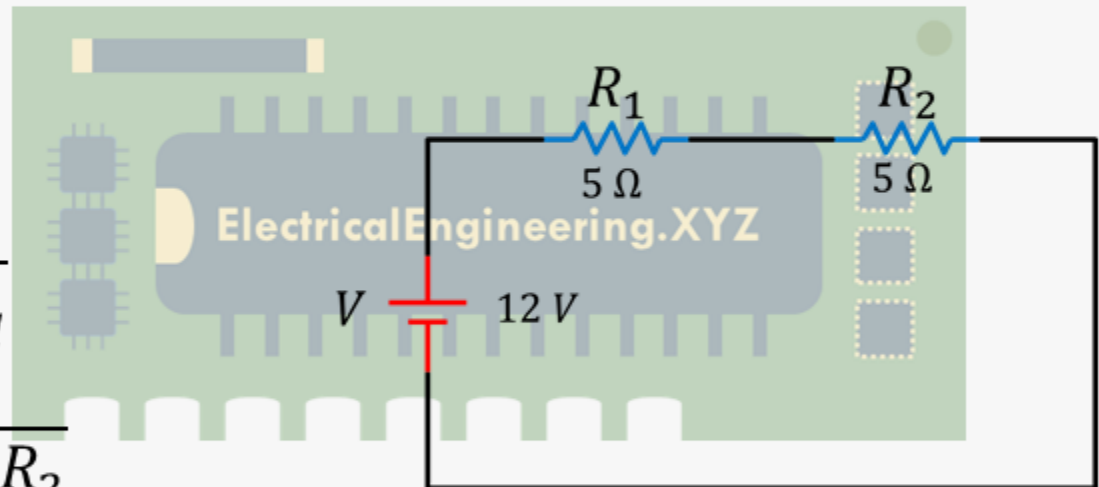
# Ohm's law for Series Circuits

Calculate the amount of current flowing through two series resistors of 5 ohms each connected to a 12 V source.

$$\begin{aligned} I &= \frac{V}{R_{eq}} \\ &= \frac{12\text{ V}}{5\ \Omega + 5\ \Omega} = \frac{12\text{ V}}{10\ \Omega} = 1.2\text{ A} \end{aligned}$$





# Ohm's law for Parallel Circuits



Calculate the amount of current flowing through two series resistors of 5 ohms each connected to a 12 V source.

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = 5 \Omega$$

$$I = \frac{V}{R_{eq}}$$

$$= \frac{12}{5 \Omega}$$


$$= 2.4 A$$

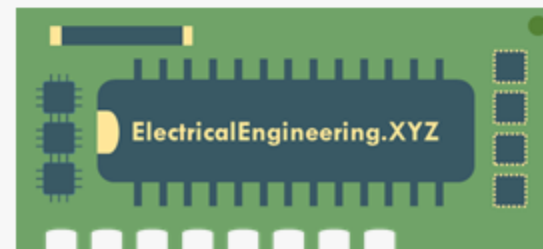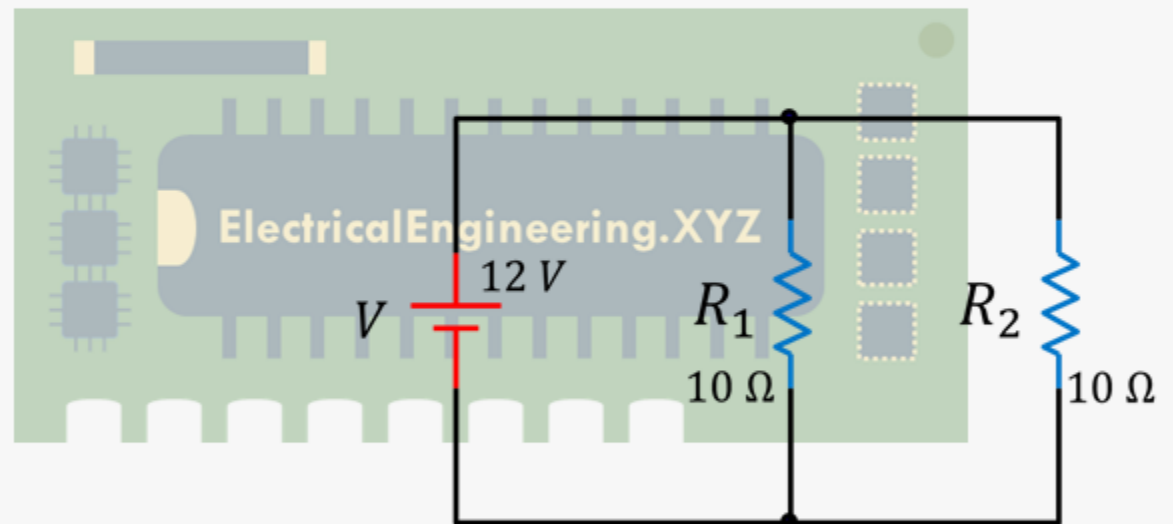


## Ohm's Law Chart

The voltage (X-axis) vs Current (Y-axis) graph plotted here for three resistors 1  $\Omega$ , 10  $\Omega$ , and 5  $\Omega$  is shown. See how the slope of graph varies with change in resistance

ElectricalEngineering.XYZ

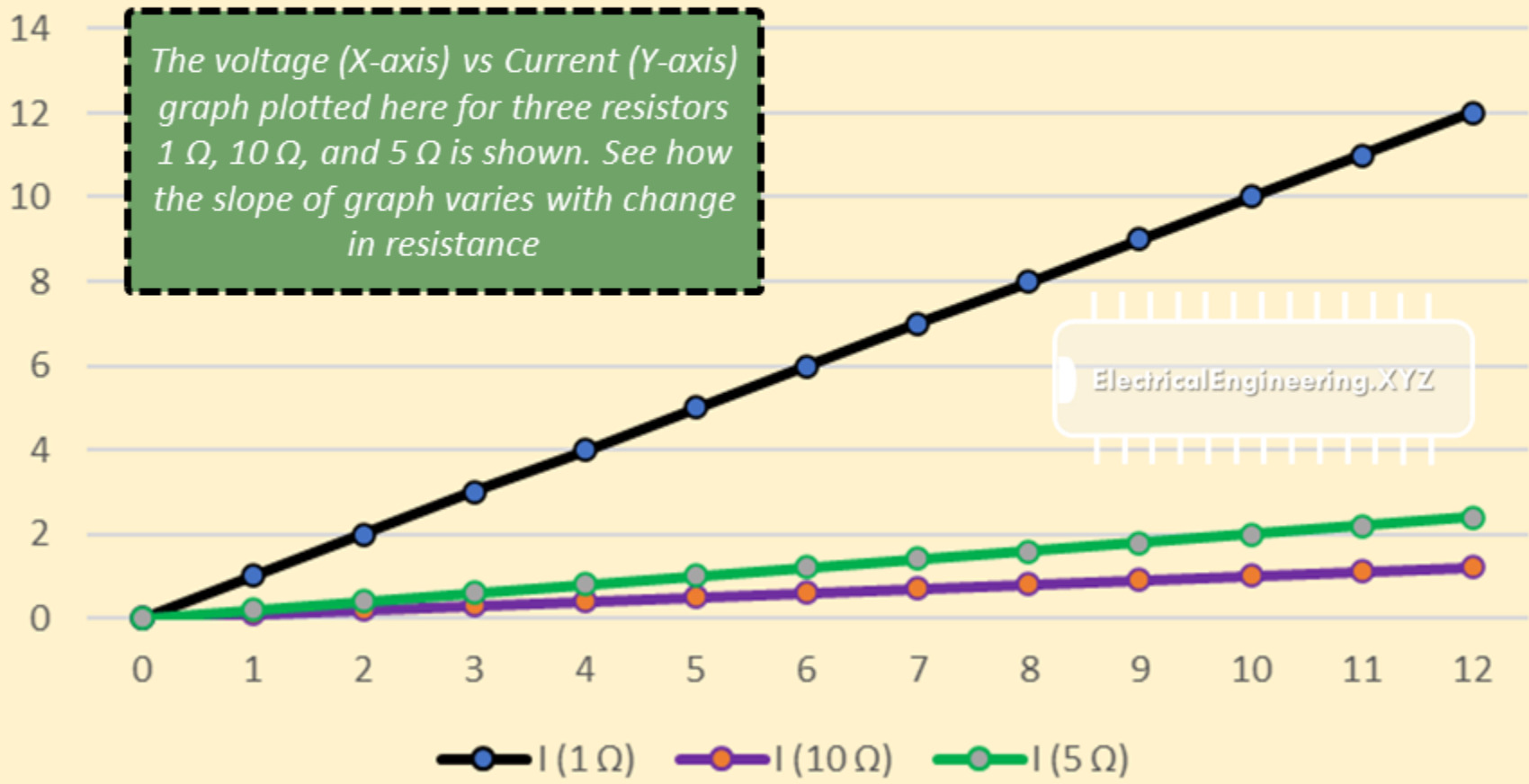

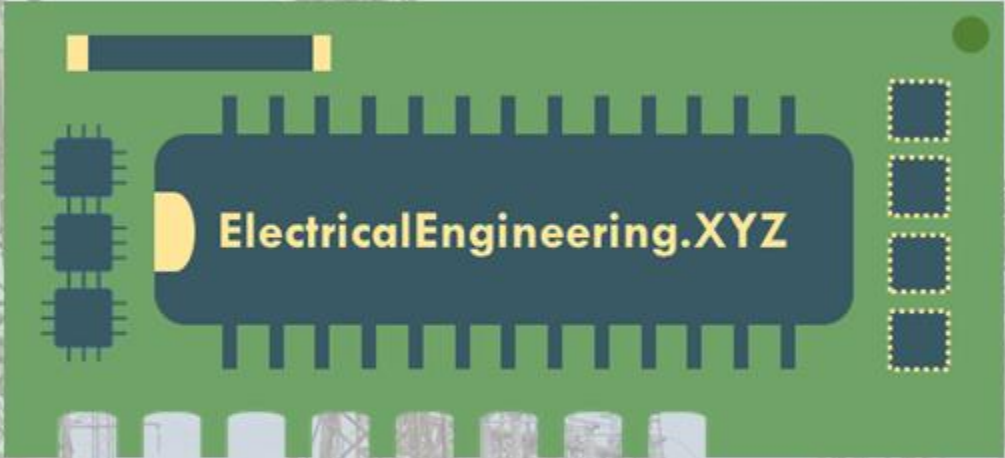

*Visit us at [www.electricalengineering.xyz](http://www.electricalengineering.xyz)*